

Laboratory Work 4 Report

ISA & Datapath Design for Multi-Cycle CPU

Mustafa BIYIK

2231454

The report consists of four main parts.

The first part is answers of the preliminary work part as hard-copy. Hardcopy contains ISA configurations and the design.

The second part is verification results of the changed modules in wvf platform of Quartus.

The third part is the simulation result of the experimental part. Testbench is applied on the Modelsim.

The last part contains the codes of the Datapath design and its testbench.

1. Preliminary Work Part(Hard-copy)

2. Verification of the modules

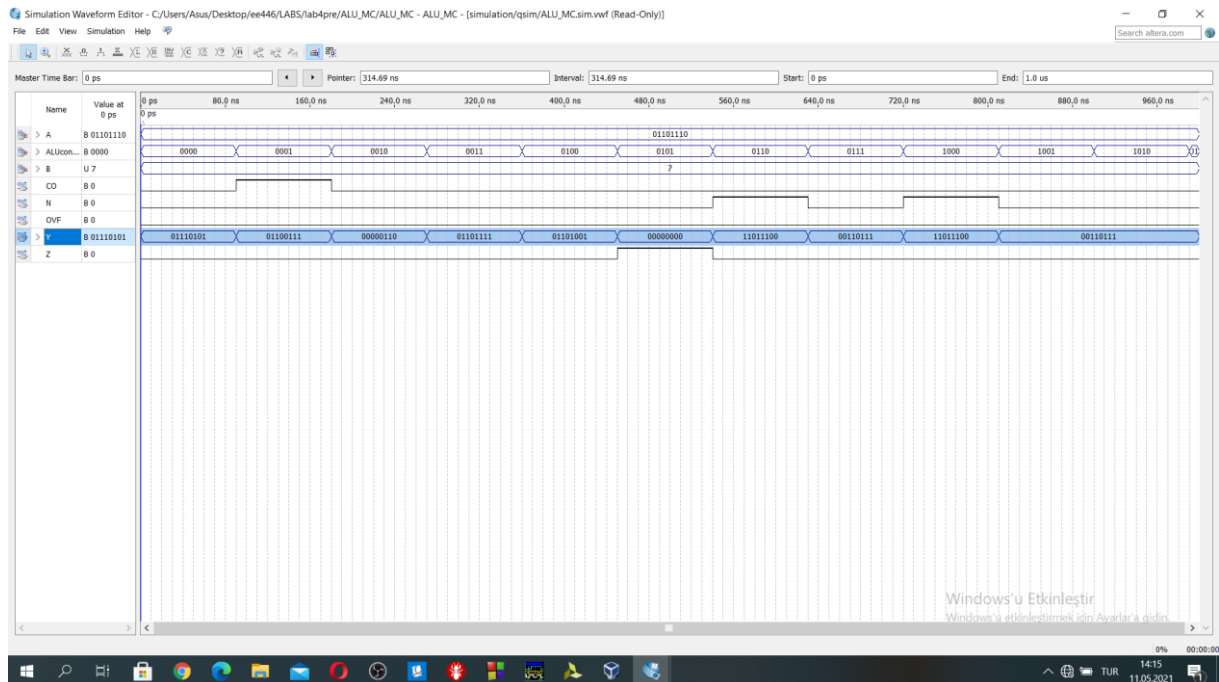


Figure 1: ALU simulation

In Figure 1, the simulation result of the ALU exists.

4'b0000: //add A (A)01101110+(B)00000111=01110101 matches with Y in the Figure 1(result)

4'b0001: //subt a-b (A)01101110-(B)00000111=01100111 matches with Y in the Figure 1(result)

4'b0010: //and (A)01101110&(B)00000111=00000110 matches with Y in the Figure 1(result)

4'b0011: //or (A)01101110|(B)00000111=01101111 matches with Y in the Figure 1(result)

4'b0100: //xor (A)01101110+(B)00000111=01101001 matches with Y in the Figure 1(result)

4'b0101: //clear clear then Y=0

4'b0110: //rol (A)01101110=11011100(Y) matches with Y in the Figure 1(result)

4'b0111: //ror (A)01101110=00110111(Y) matches with Y in the Figure 1(result)

4'b1000: //shift left lsl (A)01101110=11011100(Y) matches with Y in the Figure 1(result)

4'b1001: //shift right lsr (A)01101110=00110111(Y) matches with Y in the Figure 1(result)

4'b1010 //arithmetic shift right (A)01101110=00110111 (Y) matches with Y in the Figure 1(result)

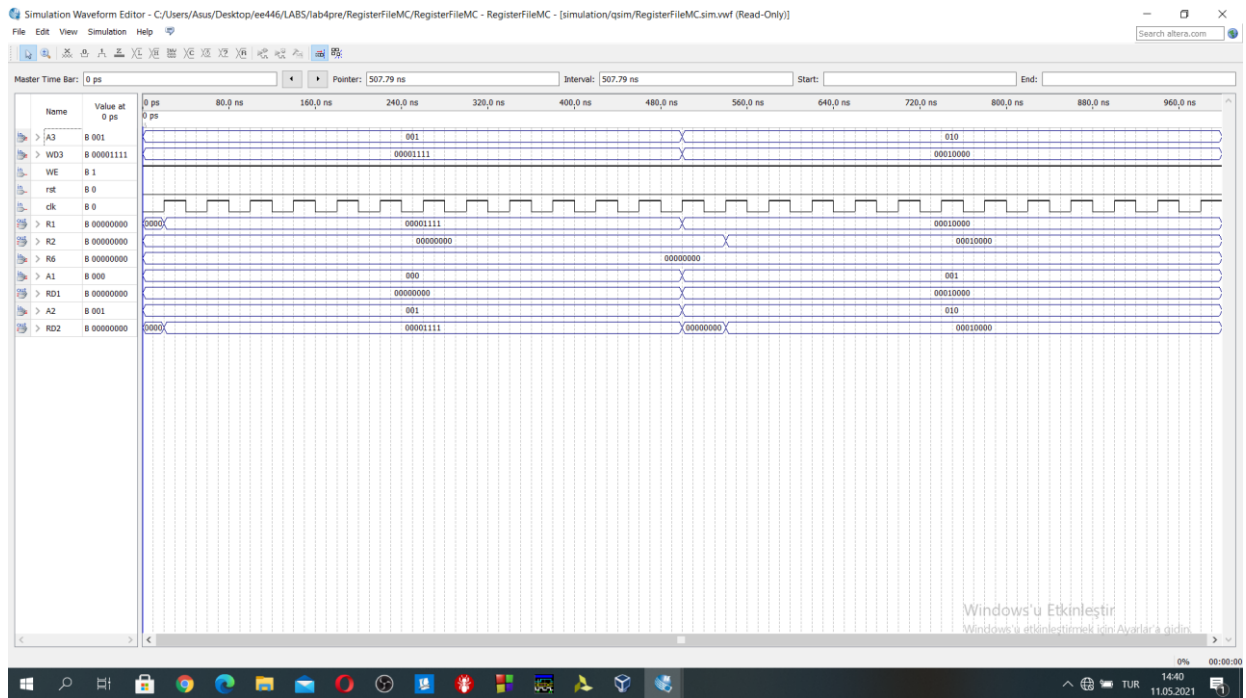


Figure 2: Register File Simulation

In Figure 2, register File for the Datapath design is designed. R1 and R2 are for the demonstration purposes. R6 is PC register. Firstly, R1(with A3) is loaded with 00001111 then the content of the R1 can be seen at the “R1” output. Also, when the A2=1, then RD2 value contains the current content of the R1 after the write operation of the R1. Then, both R1 and R2 is loaded with the 00010000 value, their value can be observed from the “R1” and “R2” outputs. They are also can be seen RD1 and RD2 when the A1 and A2 is 1 or 2.

 


Figure 3: memory read simulation

In Figure 3, memA is memory address, memRD contains the memory read output which is pointed by memA. While initializing the memory, 0,4,8... contains the instructions. 1,2,3,5,6,7,9,10,11... contains

[illegible]

Figure 4 contains the netlist of the design.

Simulation Waveform Editor - C:/Users/Asus/Desktop/ee446/LABS/lab4pre_y3/extendimmn/extendimm - extendimm - [simulation/qsim/extendimm.sim.vwf (Read-Only)]

File Edit View Simulation Help

Master Time Bar: 0 ps Pointer: 324.82 ns Interval: 324.82 ns Start: 0 ps End: 0 ps

Name	Value at 0 ps
immSrc	8 1
> instr70	8 110000000
> extend...	8 110000000

Windows'u Etkinleştir
Windows'u etkinleştirmek için Ayarlar'a gidin

When the ImmSrc=1, then input is directly served as output. When the ImmSrc=0, the last five bits of the input are extended as 8 bits by adding additional 0 to the first five bits of the input.

3. Simulation result of the Experimental work via Testbench

add-sub-and-orr-xor-clr-rol-ror-lsl-asr-lsr-ldr-ldi-str-b-bl-bi instructions in memory

```
//instructionMemory initialization
//we have 16 bits in the memORY it is used instruction
//instructions
/*
    register file initial contents
    register_R[3] = 8'b00001111; //15
    register_R[4] = 8'b00011111; //31
    register_R[5] = 8'b00111111; //63
*/

1  DATAmem[0] = 16'b0000_0001_0111_0000; //add rd 1 rn 3 rm 4
then result is " 46" initially r3=15 r4=31 r5=63
2  DATAmem[4] = 16'b0001_0010_1010_1100; //sub r2=r5-r3 "48"
3  DATAmem[8] = 16'b0010_0001_0111_0000; //and r1=r4&r3 "15"
4  DATAmem[12] = 16'b0010_1010_0111_0100; //orr r2=r3|r5 "63"
5  DATAmem[16] = 16'b0011_0001_0110_0000; //xor r1=r3^r0 "15"
because r0 initially zero
6  DATAmem[20] = 16'b0011_1010_0000_0000; //clr r2 loaded with 0

//shift operations shift rn and store it in rd
7  DATAmem[24] = 16'b0100_0001_0110_0000; //rol r1=rol r3
8  DATAmem[28] = 16'b0100_1010_1000_0000; //ror r2= ror r4
9  DATAmem[32] = 16'b0101_0001_1010_0000; //lsl r1= r5*2 126
10 DATAmem[36] = 16'b0101_1010_1000_0000; //asr r2=asr r4
11 DATAmem[40] = 16'b0110_0001_1010_0000; //lsr r1= r5/2 31

//memory instructions rd=r2
12 DATAmem[44] = 16'b1000_0010_0110_0101; //ldr r2,[r3,5]
13 DATAmem[48] = 16'b1001_0010_1111_1111; //ldi r2 255
14 DATAmem[52] = 16'b1010_0010_0110_0101; // str r2,[r3,5]
//rd=1
15 DATAmem[56] = 16'b1000_0001_0110_0101; // ldr r1,[r3,5] check
stored content

//branch instructions
16 DATAmem[60] = 16'b1100_0000_0000_1000; //b pc+8+imm8(8)=76
//B TO #76 branch here "B 76"
17 DATAmem[76] = 16'b1001_0010_0100_1100; // ldi r2 76(branch
check)

18 DATAmem[80] = 16'b1100_1000_0001_0000; //bl branch with link
to the 104

//BL TO THE 104 "BL 104"
19 DATAmem[104] = 16'b1001_0010_0110_1000; //ldi r2 104 (bl
check)

20 DATAmem[108] = 16'b1100_0000_0101_1000; //b
pc+8+imm8(64)=204

//with branch at the 108 jump here
21 DATAmem[204] = 16'b1001_0010_1101_1000; //ldi r2 216(b check)
//verify branch indirect
//BI instruction
22 DATAmem[208] = 16'b1101_0000_0000_1000; //bi r2

23 DATAmem[216] = 16'b1001_0010_1111_1111; // ldi r2 104 (bi
check)jump to here after bi instruction
//end of the instruction
```

 


Figure 6: The simulation result between 0-5000ps

As in the datamem, the first executed instruction address is 0 because PC counter value is initially. It's value increases four by four as long as PC counter does not run into branch instruction.

R1out & R2out value are used as demonstration purposes. They provide r1 and r2 values in the register file.

1st instruction ADD(four cycles)(100ps-500ps) As in the Figure 6, R1out output value is updated as 46 after four clock cycle. $r1=r3+r4 \rightarrow r1=15+31=46$, calculated value and simulation value are matching.

2nd instruction SUB(four cycles)(500ps-900ps) As in the Figure 6, R2out output value is updated as 48 after four clock cycle. $r2=r5-r3 \rightarrow r2=63-15=48$, calculated value and simulation value are matching.

3rd instruction AND(four cycles)(900ps-1300ps) As in the Figure 6, R1out output value is updated as (15)1111 after four clock cycle. $r1=r3\&r4 \rightarrow r1=00001111(15)\&00011111(31)=00001111(15)$, calculated value and simulation value are matching.

4th instruction ORR(four cycles)(1300ps-1700ps) As in the Figure 6, R2out output value is updated as (63)111111 after four clock cycle. $r2=r3\&r5 \rightarrow r2=00001111(15)\&00111111(63)=00111111(63)$, calculated value and simulation value are matching.

5th instruction XOR(four cycles)(1700ps-2100ps) As in the Figure 6, R1out output value is updated as (15)1111 after four clock cycle. $r1=r3 \wedge r0 \rightarrow r1=00001111(15) \wedge 00000000(0)=00001111(15)$, calculated value and simulation value are matching.

6th instruction CLR(four cycles)(2100ps-2500ps) As in the Figure 6, R2out output value is updated as 0 after four clock cycle. $r2 \leftarrow 0$, $\rightarrow r2 = 00000000(0)$ calculated value and simulation value are matching.

7th instruction ROL(four cycles)(2500ps-2900ps) As in the Figure 6, R1out output value is updated as (30)00011110 after four clock cycle. $r1=r3(00001111)$ rotate left by 1 $\rightarrow r1=00011110(30)$, calculated value and simulation value are matching.

8th instruction ROR(four cycles)(2900ps-3300ps) As in the Figure 6, R2out output value is updated as (143)10001111 after four clock cycle. $r2=r3(00001111)$ rotate right by 1 $\rightarrow r2=10001111(143)$, calculated value and simulation value are matching.

9th instruction LSL(four cycles)(3300ps-3700ps) As in the Figure 6, R1out output value is updated as (126)01111110 after four clock cycle. $r1=r3(00001111) \ll 1 \rightarrow r1=01111110(126)$, calculated value and simulation value are matching.

10th instruction ASR(four cycles)(3700ps-4100ps) As in the Figure 6, R2out output value is updated as (15)00001111 after four clock cycle. $r2=r4(00011111)$ arithmetic shift right by 1 $\rightarrow r2=00001111(15)$, calculated value and simulation value are matching.

11th instruction LSR(four cycles)(4100ps-4500ps) As in the Figure 6, R1out output value is updated as (31)00011111 after four clock cycle. $r1=r5(00111111) \gg 1 \rightarrow r1=00011111(31)$, calculated value and simulation value are matching.

12th instruction LDR(five cycles)(4500ps-5000ps) As in the Figure 6, R2out output value is updated as 0 after five clock cycle. $\text{ldr } r2, [r3, \#5] \rightarrow r2$ is loaded with data at the memory address 20. The data is equal to 0 at pointed by the address. Calculated value and simulation value are matching. Why it is 0, because imm8 is 0000 0000.

 


Figure 7: The simulation result between 5000ps-9000ps

13th instruction LDI(three cycles)(5000ps-5300ps) As in the Figure 7, R2out output value is updated as 255(1111 1111) after three clock cycle. imm8 value is moved to the r2 register. The moved value can be observed from Figure 7. Calculated value and simulation value are matching.

14th instruction STR(four cycles)(5300ps-5700ps) As in the Figure 7, str r2,[r3,5] → r2 is stored to the "[r3]+5" address as 0000 0000 1111 1111.

```
//checking STR with LDR
```

15th instruction LDR (five cycles) (5700ps-6200ps) As in the Figure 7, R1out output value is updated as 255 after five clock cycle. `Ldr r1,[r3,5]` → r1 is loaded with data at the memory address 20. The data is equal to 255 at pointed by the address. Calculated value and simulation value are matching.

16th instruction B(branch)(three cycles)(6200ps-6500ps). When we look at the instruction memory, imm8 bits of the branch are 0000 1000(8), the next executed instruction must be PC+8+imm8. Current PC counter value is equal to 60. The next instruction must be at the address value 76.

Note: In my design, I do not multiply immediate with 4.

```
//check Branch working or not,
```

//imm8 value is equal to branched PC counter value. Then it's value is moved to the r2 as 76.

17th instruction LDI(three cycles)(6500ps-6800ps) As in the Figure 7, R2out output value is updated as 76(0100 1100) after three clock cycle. imm8 value is moved to the r2 register. The moved value can be observed from Figure 7. Calculated value and simulation value are matching.

Figure 8: overall simulation result which includes memory, data-processing, shift and some branch (b, bl, bi) instructions

Additional demonstration parts for the BEQ,BNE,BNC,BC

```
//B TO #76 branch here "B 76"
    DATAmem[76] = 16'b1001_0010_0100_1100; //ldi r2 76
    DATAmem[80] = 16'b1100_1000_0001_0000; //bl branch with link
to the 104

    //BL TO THE 104 "BL 104"
    DATAmem[104] = 16'b1001_0010_0110_1000; //ldi r2 104
    DATAmem[108] = 16'b0001_0001_1011_0100; //sub r1=r5-r5 0
    DATAmem[112] = 16'b1101_1000_0000_1000; //beq then branch 128
//equal then branch here "BEQ 128" 128
    DATAmem[128] = 16'b1001_0010_1000_0000; //ldi r2 128
    DATAmem[132] = 16'b0001_0001_1010_1100; //sub r1=r5-r3 not
equal

    DATAmem[136] = 16'b1110_0000_0000_1000; //bne then branch 152

    //not equal then "BNE 152" to 152
    DATAmem[152] = 16'b1001_0010_1001_1000; //ldi r2 152
    DATAmem[156] = 16'b0001_0001_1010_1100; //sub r1=r5-r3 not
equal

    DATAmem[160] = 16'b1111_0000_0000_1000; //bnc

    //branch "BNC 176" 176 if the carry flag is 0
    DATAmem[176] = 16'b1001_0010_1011_0000; //ldi r2 176
    DATAmem[180] = 16'b0000_0001_0100_1000; //add rd 1 rn 2 rm
2 initially r2=176
    DATAmem[184] = 16'b1110_1000_0000_1000; //bc if carry flag
is set


    //bc control "BC 200"
    DATAmem[200] = 16'b1001_0010_1100_1000; //ldi r2 200

    DATAmem[204] = 16'b1001_0010_1101_1000; //ldi r2 216
```

After the discussion in the ODTUclass, some part of the instruction memory excluded. I add also BNC, BC, BEQ, BNE. I have controlled just the flags in testbench. I follow the similar steps while verifying previous testbench. Firstly, I use branch instruction, then I have demonstrated with LDI instructions.

Instruction at 108 activates the 0 flag. The beq branch works. The PC jumps to the address 128 in this address r2 is loaded with 128 as seen in Figure 9. R2 value is equal to 128 at time 9500 ps. That means BEQ works perfectly.

 Instruction at 132 does not activate 0 flag. BNE works. The PC jumps to the address 152 in this address r2 is loaded with 152 as seen in Figure 9. R2 value is equal to 152 at time 10500 ps. That means BNE works perfectly.



4. Datapath design Code and Testbench code